

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
Fourth Semester B.Tech Degree Examination June 2022 (2019 scheme)

Course Code: ECT202

Course Name: ANALOG CIRCUITS

Max. Marks: 100

Duration: 3 Hours

**PART A***(Answer all questions; each question carries 3 marks)*

Marks

- |    |   |   |
|----|---|---|
| 1  | Draw the circuit of an RC integrator. Give the conditions for an RC circuit to act as integrator.                           | 3 |
| 2  | Define Stability factor. Derive the expression for stability factor 'S'.  | 3 |
| 3  | Differentiate between dc and ac load lines.   | 3 |
| 4  | What is the significance of Miller effect on high frequency amplifiers?   | 3 |
| 5  | Given $K=0.4\text{mA/V}^2$ and $I_{D(ON)} = 3.5\text{mA}$ with $V_{GS(ON)} = 4\text{V}$ . Determine the value of $V_{TH}$ . | 3 |
| 6  | What are the effects of cascading in gain and bandwidth of an amplifier?  | 3 |
| 7  | Differentiate positive feedback and negative feedback.  | 3 |
| 8  | Draw the block diagrams of current series and current shunt feedback.   | 3 |
| 9  | Illustrate the principle of output current boosting circuit in a voltage regulator?   | 3 |
| 10 | What do you mean by crossover distortion? How can it be eliminated?   | 3 |


**PART B***(Answer one full question from each module, each question carries 14 marks)***Module -1**

- Given an input wave,  $V_{in}=10\sin\omega t$ . Setup and explain a clamper that clamps
- |    |  |   |
|----|--|---|
| 11 | a) the wave to 22.3V at the positive peak, assuming a voltage drop of 0.7 V across the diode. Draw the output waveform and transfer characteristics also.  | 8 |
| 12 | b) Design a fixed bias circuit for a CE amplifier such that operating point is $V_{CE} = 8\text{V}$ and $I_C = 2\text{mA}$ . Given, a fixed 15V d.c. supply and a silicon transistor with $\beta = 100$ . Take base-emitter voltage $V_{BE} = 0.6\text{V}$ and neglect $R_E$ . | 6 |
| 12 | a) With necessary diagrams, explain any two biasing methods of BJT.  | 8 |
|    | b) Set up and explain a slicer circuit that clips an input sine wave at +2V and +4V.   | 6 |
|    | b) Draw the transfer characteristics.  |   |

## Module -2

- 13 a) Analyse the high frequency response of an amplifier in CE configuration using hybrid  $\pi$  model. 8
- b) Draw and explain the frequency response of RC coupled amplifier. 6
- Using hybrid  $\pi$  model, calculate the small signal voltage gain, input impedance and output impedance of the given circuit.
- Given,  $V_{BE}=0.7V$ ,  $V_A=80V$ ,  $I_c = 2mA$  and  $\beta=100$ . (Neglecting  $r_o$ )

14

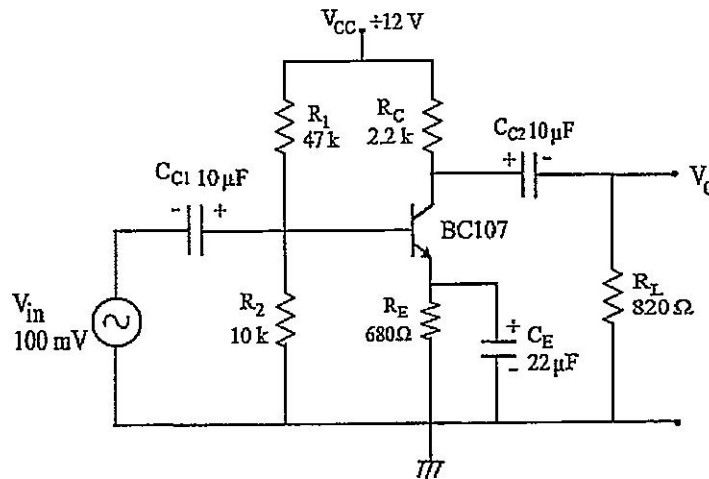


14

## Module -3

- a) Draw the CS stage with diode connected load and deduce the expression for voltage gain of the amplifier. 8
- Calculate the drain current and drain-to-source voltage of a common source circuit with an n-channel enhancement mode MOSFET. Find the power dissipated in the transistor.
- $R_1=22K\Omega$ ,  $R_2=10K\Omega$ ,  $R_D=6.8K\Omega$ ,  $V_{DD}=8V$ ,  $V_T=1V$ ,  $K_n=0.1mA/V^2$

15

b)

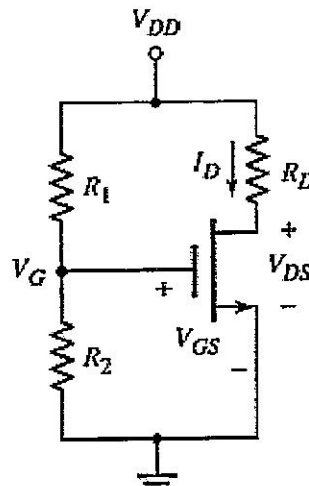

6

- Draw the circuit of a common source amplifier using MOSFET. Derive the
- 16 a) expressions for voltage gain, input resistance and output resistance from small signal equivalent circuit. 8
- b) Briefly explain a Cascode amplifier. 6

**Module -4**

- With neat circuit diagram, explain the discrete BJT circuit in voltage-series feedback and derive the expression for voltage gain, input impedance and output impedance. 14
- 17
- 18 a) Design wein-bridge oscillator using BJT to generate 1KHz sine wave. 9
- b) With neat circuit diagram, explain the working of Hartley oscillator 5

**Module -5**

- What are the factors affecting the variation in output voltage of voltage regulator? With a circuit diagram, explain how load and line regulations are achieved in a shunt voltage regulator. 14
- 19
- 20 Explain the working of Class B push-pull power amplifier with a neat circuit diagram and output waveforms. Derive the expression for collector efficiency. 14

\*\*\*

